




SACRAMENTO
STATE




Account




Dashboard




Courses




Calendar

 

Inbox



Help



- Spring 2019
- Home
- Announcements
- Assignments
- Discussions
- Grades
- People
- Files
- Syllabus
- Quizzes
- Modules
- Collaborations
- Blackboard Collaborate
- Office 365
- Follett Discover
- Smarthinking Online Tutoring
- StudyMate
- Zoom

Project 1

Re-submit Assignment

Due Apr 1 by 11:59pm Points 100 Submitting a file upload

Project 2: Design a 3-bit Carry Propagate Addder (CPA) Structural Model

Design and simulate a structural model (not behavioral) of a 3-bit CPA adder. Follow the steps below but make sure you read the entire assignment before you start. Refer to Homework 4 and Chapter 2 for examples of structural models and structural circuit models. You are allowed to work in groups of 2 but you could work alone if you choose to.

1. Structural model of CPA:

Design a 3-bit CPA adder as follows:

First, create a structural model of a 1-bit Full Addder (refer to homework 4) and instantiate it 3 times inside your 3-bit CPA module and make the necessary wire connections. To instantiate the Full addder module, you need to add an ``include` line on top of your CPA Verilog module.

Your module ports (inputs and outputs), should be as follow:

```
`include full_adderv
module adder_3bits
(
    input [2:0] a, b,
    input cin,
    output [2:0] sum,
    output co
);
```

2. Create a test bench to test the following cases:

```
a = 3'b001 b = 3'b001 cin = 1'b0
a = 3'b011 b = 3'b010 cin = 1'b1
a = 3'b011 b = 3'b100 cin = 1'b0
a = 3'b111 b = 3'b001 cin = 1'b0
```

Your test bench should clearly display the inputs and output results.

Refer to Homework 4 and the textbook to create a Verilog testbench module and enter the above test cases as test vectors. Note, you must simulate to get outputs from your Verilog model.

3. Each student must submit individually to Canvas

- a) Verilog models of Full Addder, Carry Propagate Addder (CPA) and Testbench.
- c) The executable created during compilation "simv"
- b) The screenshot of your simulation results.

Submission

✓ Submitted!

- Apr 1 at 12:36am
- [Submission Details](#)
- [Download adder_3bits_tb.v](#)
- [Download adder_3bitsv](#)
- [Download fullAdderv](#)
- [Download simv-1](#)
- [Download compile.png](#)
- [Download outfile_result.png](#)

Grade: 100% (100 pts possible)
Graded Anonymously: no

Comments:
No Comments